 



$$\begin{array}{r}
 6_{10} = 1 \\
 + 7_{10} = 1 \\
 \hline
 \end{array}
 \begin{array}{r}
 4\text{er} \\
 1 \\
 \downarrow \text{A} \\
 1 \\
 \downarrow \text{B}
 \end{array}$$



8er 4er

Volladdierer

 
$$\begin{array}{r}
 2\text{er} \\
 1 \\
 \downarrow \text{A} \\
 1 \\
 \downarrow \text{B}
 \end{array}$$



2er

Volladdierer
 
$$\begin{array}{r}
 1\text{er} \\
 0 \\
 \downarrow \text{A} \\
 1 \\
 \downarrow \text{B}
 \end{array}$$



1er

Halbaddierer